

# Lab Content

## Course: CSE3112 (Computer Architecture and Organization Lab)



### • Experiment 1

<b>Title</b>	<b>Synchronous Data Transfer</b>
<b>Outline</b>	<ul style="list-style-type: none"> <li>• To design and implement a digital circuit to transfer data serially</li> <li>• At the sender end the parallel data is converted to serial data to transfer the data to receiver using a single data line.</li> <li>• At the receiver end the serial data will be reconstructed to its parallel form.</li> <li>• Both sender and receiver circuits should be synchronized using a single clock.</li> </ul>
<b>Apparatus</b>	<ul style="list-style-type: none"> <li>• 4-bit Binary Counter, 74LS161</li> <li>• 8-input Multiplexer, 74LS151</li> <li>• 8-bit Serial-in Parallel-out Shift Register, 74LS164</li> <li>• Octal D-type Flip-Flop, 74LS374</li> <li>• Hex Inverter, 74LS04</li> <li>• Digital IC Trainer</li> </ul>
<b>Circuit Diagram</b>	
<b>Task</b>	<ul style="list-style-type: none"> <li>• Design of the digital circuit</li> <li>• Implementation of the design</li> <li>• Testing of the circuit</li> <li>• Report writing             <ul style="list-style-type: none"> <li>○ Name of the experiment</li> <li>○ Objective</li> <li>○ Apparatus</li> <li>○ Design of the circuit                 <ul style="list-style-type: none"> <li>▪ Detail design methodology</li> <li>▪ Truth table (if required)</li> </ul> </li> <li>○ Circuit Diagram</li> <li>○ Experimental data</li> <li>○ Result and discussion</li> <li>○ Precautions</li> </ul> </li> </ul>
<b>Mode of Evaluation</b>	<b>Experiment, Viva and Report</b>
<b>Percentage of Weight</b>	<b>16%</b>

## • Experiment 2

Title	Memory operations																
Outline	<ul style="list-style-type: none"> <li>To design and implement a memory subsystem to store data in memory and then display the stored data into LED</li> <li>Writing the following data into corresponding memory addresses using synchronized counter</li> </ul> <table border="1"> <thead> <tr> <th>Address</th><th>Data</th></tr> </thead> <tbody> <tr> <td>60</td><td>F0</td></tr> <tr> <td>61</td><td>E1</td></tr> <tr> <td>62</td><td>D2</td></tr> <tr> <td>.</td><td>.</td></tr> <tr> <td>.</td><td>.</td></tr> <tr> <td>.</td><td>.</td></tr> <tr> <td>6F</td><td>0F</td></tr> </tbody> </table> <ul style="list-style-type: none"> <li>Display the stored data into LED</li> </ul>	Address	Data	60	F0	61	E1	62	D2	.	.	.	.	.	.	6F	0F
Address	Data																
60	F0																
61	E1																
62	D2																
.	.																
.	.																
.	.																
6F	0F																
Apparatus	<ul style="list-style-type: none"> <li>4-bit Binary Counter, 74LS161</li> <li>Static RAM, 6116</li> <li>Hex Inverter, 74LS04</li> <li>Digital IC Trainer</li> </ul>																

### Circuit Diagram

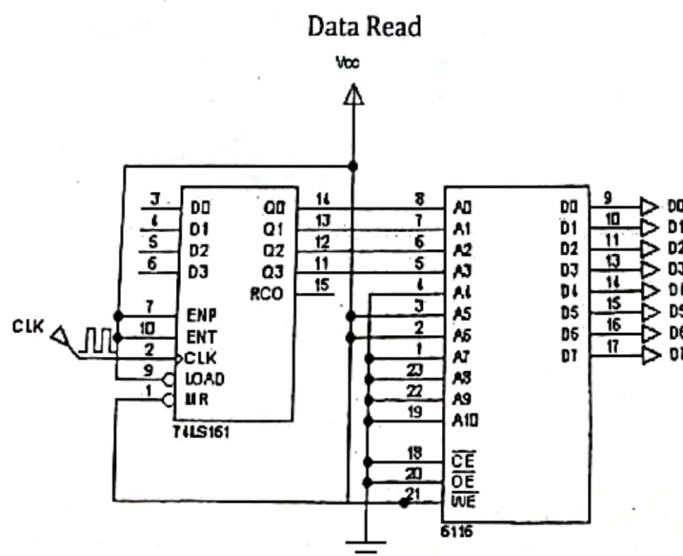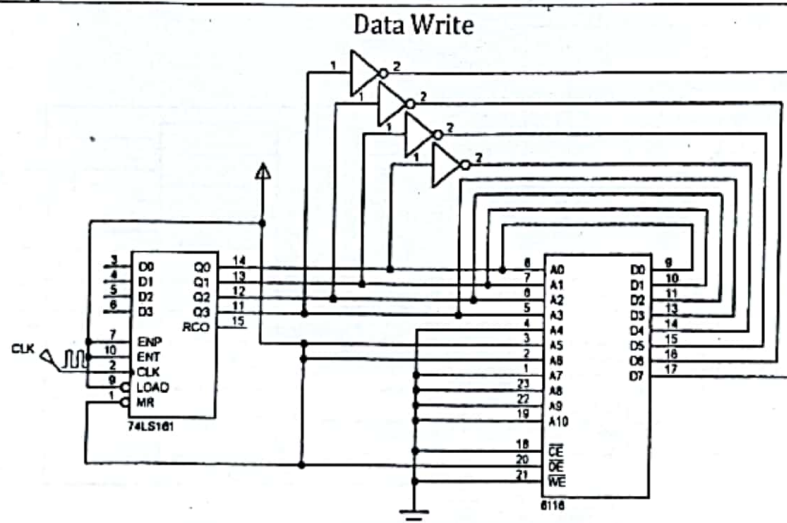


Task	<ul style="list-style-type: none"> <li>• Design of the digital circuit</li> <li>• Implementation of the design</li> <li>• Testing the circuit</li> <li>• Report writing               <ul style="list-style-type: none"> <li>○ Name of the experiment</li> <li>○ Objective</li> <li>○ Apparatus</li> <li>○ Design of the circuit                   <ul style="list-style-type: none"> <li>▪ Detail design methodology</li> <li>▪ Truth table (if required)</li> </ul> </li> <li>○ Circuit Diagram</li> <li>○ Experimental data</li> <li>○ Result and discussion</li> <li>○ Precautions</li> </ul> </li> </ul>
Mode of Evaluation	Experiment, Viva and Report
Percentage of Weight	15%

### • Experiment 3

Title	Frequency counter
Outline	<ul style="list-style-type: none"> <li>• To design and implement a frequency counter. The input frequency will be divided by a constant divisor N (<math>N=1, 2, \dots, 15</math>) before feeding it to desired frequency counter. The output of the frequency counter should be show on a 7-segment display</li> <li>• Design a circuit for dividing the input frequency by a constant divisor N, where N is integer and variable. <u>N should be easily changeable.</u></li> <li>• Design a circuit to count frequency and show the output on a 7-segment display.</li> </ul>
Task	<ul style="list-style-type: none"> <li>• Design of the digital circuit</li> <li>• Implementation of the design</li> <li>• Testing the circuit</li> <li>• Report writing               <ul style="list-style-type: none"> <li>○ Name of the experiment</li> <li>○ Objective</li> <li>○ Apparatus</li> <li>○ Design of the circuit                   <ul style="list-style-type: none"> <li>▪ Detail design methodology</li> <li>▪ Truth table (if required)</li> </ul> </li> <li>○ Circuit Diagram</li> <li>○ Experimental data</li> <li>○ Result and discussion</li> <li>○ Precautions</li> </ul> </li> </ul>



# Circuit Diagram

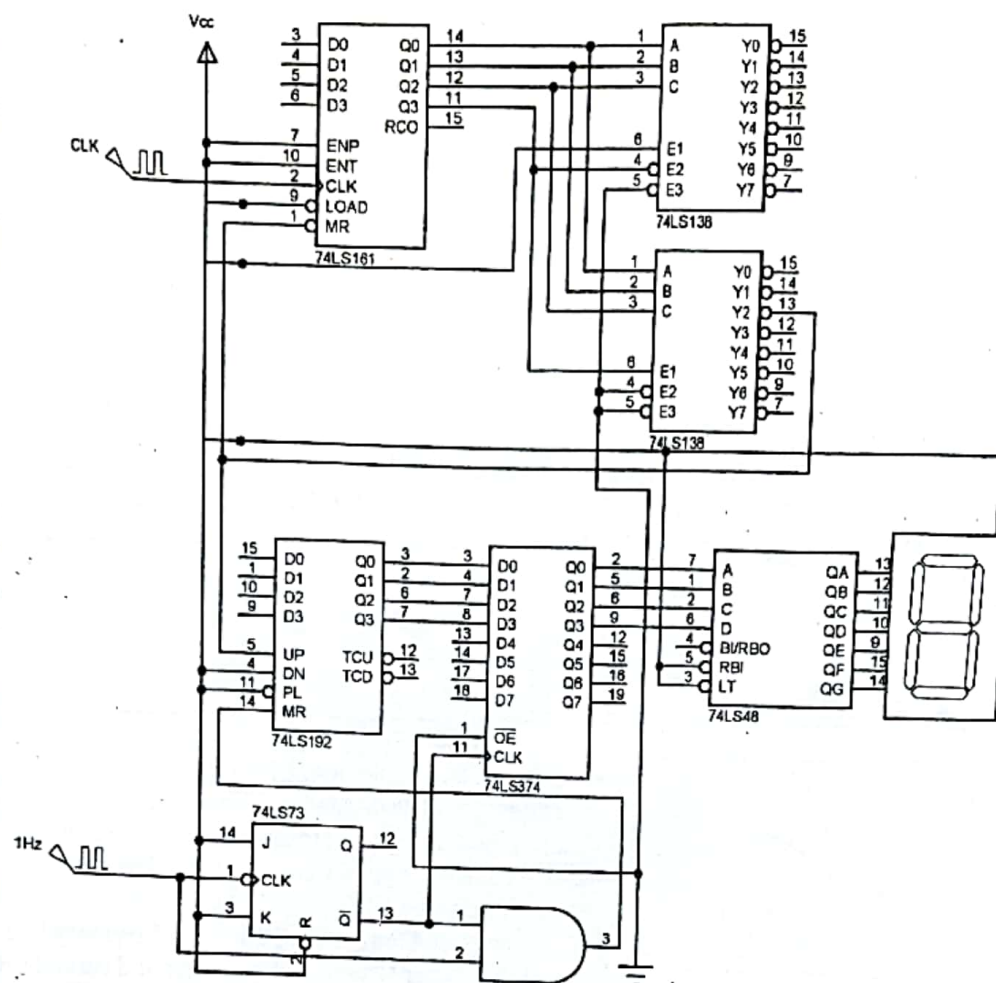

## Apparatus

- 4-bit Binary Counter, 74LS161
- 3 to 8 line Decoder, 74LS138
- 4-bit BCD Counter, 74LS191
- Dual J-K Flip-Flop, 74LS76
- Quad 2-input AND gate, 74LS08
- Octal D-type Flip-Flop, 74LS374
- BCD to 7-Segment Decoder, 74LS47
- 7-Segment Display LED
- Digital IC Trainer

## Mode of Evaluation

Experiment, Viva and Report

## Percentage of Weight

19%


# • Experiment 4

<b>Title</b>	Analog to Digital Conversion
<b>Outline</b>	<ul style="list-style-type: none"> <li>• To design and implement a circuit to convert analog signal (potential difference) into digital data by using an Analog to Digital Converter than store the data in a latch and display the converted digital data using LED</li> <li>• Design a circuit with controls to initialize the conversion process.</li> <li>• Decode port if multiple input analog input lines available on ADC IC and required to digitize multiple analog input signals.</li> <li>• Design circuit to store digital signal in a latch automatically. (Required to synchronized with ADC IC)</li> </ul>
<b>Apparatus</b>	<ul style="list-style-type: none"> <li>• 8-bit <math>\mu</math>P Compatible A/D Converter ADC0809</li> <li>• Octal D-type Latch, 74LS373</li> <li>• Digital IC Trainer</li> </ul>
<b>Circuit Diagram</b>	<p>The diagram illustrates the circuit for converting an analog signal to digital. The ADC0809 is connected to a DC source (0V-5V) for its inputs. A single pulse is connected to the START pin. The output of the ADC (D0-D7) is connected to the inputs of the 74LS373 latch. The latch is enabled by the VCC (5V) and its output is connected to the 8-bit LED display.</p>
<b>Task</b>	<ul style="list-style-type: none"> <li>• Design of the digital circuit</li> <li>• Implementation of the design</li> <li>• Testing the circuit</li> <li>• Report writing <ul style="list-style-type: none"> <li>◦ Name of the experiment</li> <li>◦ Objective</li> <li>◦ Apparatus</li> <li>◦ Design of the circuit <ul style="list-style-type: none"> <li>▪ Detail design methodology</li> <li>▪ Truth table (if required)</li> </ul> </li> <li>◦ Circuit Diagram</li> <li>◦ Experimental data</li> <li>◦ Result and discussion</li> <li>◦ Precautions</li> </ul> </li> </ul>
<b>Mode of Evaluation</b>	Experiment, Viva and Report
<b>Percentage of Weight</b>	14%

# • Experiment 5

Title	Arithmetic circuit control design																																																																																																												
Outline	<ul style="list-style-type: none"> <li>To design and implement arithmetic circuits with selection variable <math>S_0</math> &amp; <math>S_1</math> and operand A (4 bits), B (4 bits) &amp; <math>C_{in}</math> that generates the following operations:</li> </ul> <table> <tr> <th><math>S_0</math></th><th><math>S_1</math></th><th><math>C_{in}=0</math></th><th><math>C_{in}=1</math></th></tr> <tr> <td>0</td><td>0</td><td><math>F=A+B</math></td><td><math>F=A+B+1</math></td></tr> <tr> <td>0</td><td>1</td><td><math>F=A</math></td><td><math>F=A+1</math></td></tr> <tr> <td>1</td><td>0</td><td><math>F=B'</math></td><td><math>F=B'+1</math></td></tr> <tr> <td>1</td><td>1</td><td><math>F=A+B'</math></td><td><math>F=A+B'+1</math></td></tr> </table> <ul style="list-style-type: none"> <li>Construct truth table and K-Map to generate Boolean equations for the arithmetic circuit.</li> <li>Implement the circuit for according to the Boolean equations.</li> </ul>	$S_0$	$S_1$	$C_{in}=0$	$C_{in}=1$	0	0	$F=A+B$	$F=A+B+1$	0	1	$F=A$	$F=A+1$	1	0	$F=B'$	$F=B'+1$	1	1	$F=A+B'$	$F=A+B'+1$																																																																																								
$S_0$	$S_1$	$C_{in}=0$	$C_{in}=1$																																																																																																										
0	0	$F=A+B$	$F=A+B+1$																																																																																																										
0	1	$F=A$	$F=A+1$																																																																																																										
1	0	$F=B'$	$F=B'+1$																																																																																																										
1	1	$F=A+B'$	$F=A+B'+1$																																																																																																										
Apparatus	<ul style="list-style-type: none"> <li>4-bit Binary Full Adder, 74LS283</li> <li>Quad 2-input AND gate, 74LS08</li> <li>Quad 2-input OR gate, 74LS32</li> <li>Hex Inverter, 74LS04</li> <li>Quad 2-input Exclusive-OR gate, 74LS86</li> <li>Digital IC Trainer</li> </ul>																																																																																																												
Truth Table	<table> <tr> <th colspan="4">Input</th><th colspan="2">Output</th></tr> <tr> <th><math>S_0</math></th><th><math>S_1</math></th><th><math>A_i</math></th><th><math>B_i</math></th><th><math>X_i</math></th><th><math>Y_i</math></th></tr> <tr><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>0</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>1</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>1</td><td>1</td><td>0</td></tr> </table>	Input				Output		$S_0$	$S_1$	$A_i$	$B_i$	$X_i$	$Y_i$	0	0	0	0	0	0	0	0	0	1	0	1	0	0	1	0	1	0	0	0	1	1	1	1	0	1	0	0	0	0	0	1	0	1	0	0	0	1	1	0	1	0	0	1	1	1	1	0	1	0	0	0	0	1	1	0	0	1	0	0	1	0	1	0	0	1	1	0	1	1	0	0	1	1	0	0	0	1	1	1	0	1	0	0	1	1	1	0	1	1	1	1	1	1	1	0
Input				Output																																																																																																									
$S_0$	$S_1$	$A_i$	$B_i$	$X_i$	$Y_i$																																																																																																								
0	0	0	0	0	0																																																																																																								
0	0	0	1	0	1																																																																																																								
0	0	1	0	1	0																																																																																																								
0	0	1	1	1	1																																																																																																								
0	1	0	0	0	0																																																																																																								
0	1	0	1	0	0																																																																																																								
0	1	1	0	1	0																																																																																																								
0	1	1	1	1	0																																																																																																								
1	0	0	0	0	1																																																																																																								
1	0	0	1	0	0																																																																																																								
1	0	1	0	0	1																																																																																																								
1	0	1	1	0	0																																																																																																								
1	1	0	0	0	1																																																																																																								
1	1	0	1	0	0																																																																																																								
1	1	1	0	1	1																																																																																																								
1	1	1	1	1	0																																																																																																								
K-Map	<p><math>X_i</math>:</p> <table> <tr> <th></th><th><math>S_0'S_1'</math></th><th><math>S_0'S_1</math></th><th><math>S_0S_1</math></th><th><math>S_0S_1'</math></th></tr> <tr> <td><math>A_i'B_i'</math></td><td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr> <td><math>A_i'B_i</math></td><td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr> <td><math>A_iB_i</math></td><td>1</td><td>1</td><td>1</td><td>0</td></tr> <tr> <td><math>A_iB_i'</math></td><td>1</td><td>1</td><td>1</td><td>0</td></tr> </table> $X_i = (S_0' + S_1)A_i$ <p><math>Y_i</math>:</p> <table> <tr> <th></th><th><math>S_0'S_1'</math></th><th><math>S_0'S_1</math></th><th><math>S_0S_1</math></th><th><math>S_0S_1'</math></th></tr> <tr> <td><math>A_i'B_i'</math></td><td>0</td><td>0</td><td>1</td><td>1</td></tr> <tr> <td><math>A_i'B_i</math></td><td>1</td><td>1</td><td>0</td><td>0</td></tr> <tr> <td><math>A_iB_i</math></td><td>1</td><td>1</td><td>0</td><td>0</td></tr> <tr> <td><math>A_iB_i'</math></td><td>0</td><td>0</td><td>1</td><td>1</td></tr> </table> $Y_i = (S_0 + S_1')(B_i \oplus S_0)$		$S_0'S_1'$	$S_0'S_1$	$S_0S_1$	$S_0S_1'$	$A_i'B_i'$	0	0	0	0	$A_i'B_i$	0	0	0	0	$A_iB_i$	1	1	1	0	$A_iB_i'$	1	1	1	0		$S_0'S_1'$	$S_0'S_1$	$S_0S_1$	$S_0S_1'$	$A_i'B_i'$	0	0	1	1	$A_i'B_i$	1	1	0	0	$A_iB_i$	1	1	0	0	$A_iB_i'$	0	0	1	1																																																										
	$S_0'S_1'$	$S_0'S_1$	$S_0S_1$	$S_0S_1'$																																																																																																									
$A_i'B_i'$	0	0	0	0																																																																																																									
$A_i'B_i$	0	0	0	0																																																																																																									
$A_iB_i$	1	1	1	0																																																																																																									
$A_iB_i'$	1	1	1	0																																																																																																									
	$S_0'S_1'$	$S_0'S_1$	$S_0S_1$	$S_0S_1'$																																																																																																									
$A_i'B_i'$	0	0	1	1																																																																																																									
$A_i'B_i$	1	1	0	0																																																																																																									
$A_iB_i$	1	1	0	0																																																																																																									
$A_iB_i'$	0	0	1	1																																																																																																									

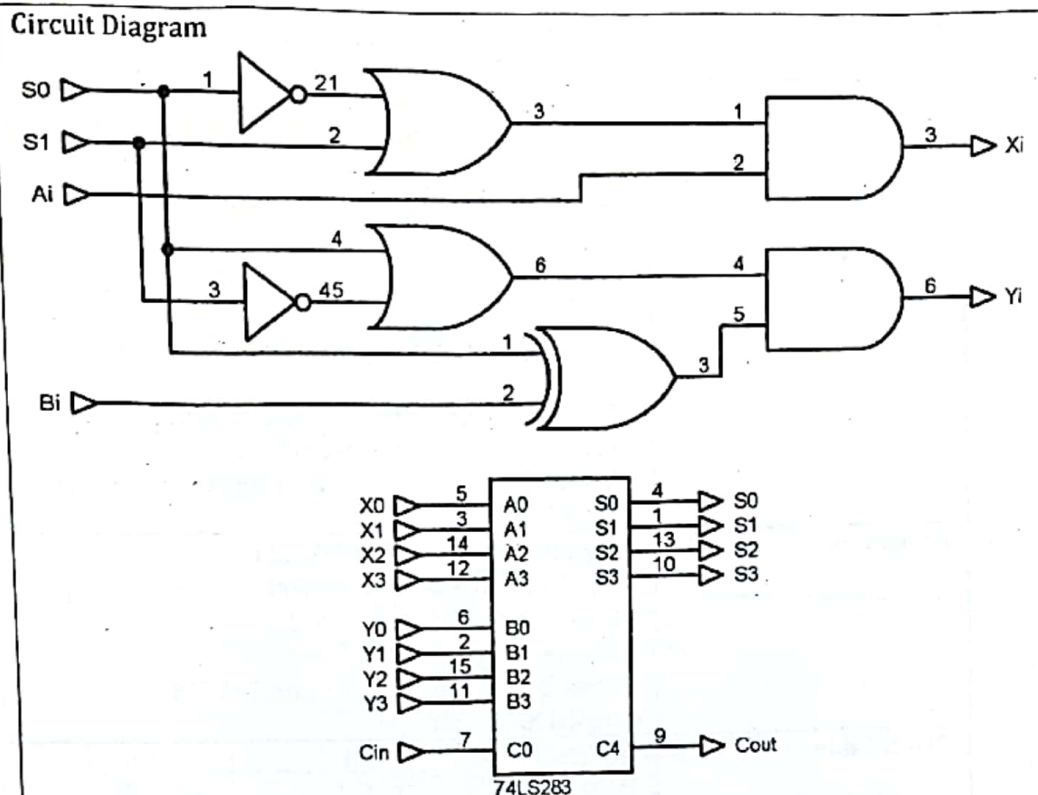CSE-3112(Computer Architecture and Organization Lab)





<b>Task</b>	<ul style="list-style-type: none"> <li>• Design of the digital circuit</li> <li>• Implementation of the design</li> <li>• Testing the circuit</li> <li>• Report writing               <ul style="list-style-type: none"> <li>◦ Name of the experiment</li> <li>◦ Objective</li> <li>◦ Apparatus</li> <li>◦ Design of the circuit                   <ul style="list-style-type: none"> <li>▪ Detail design methodology</li> <li>▪ Truth table (if required)</li> </ul> </li> <li>◦ Circuit Diagram</li> <li>◦ Experimental data</li> <li>◦ Result and discussion</li> <li>◦ Precautions</li> </ul> </li> </ul>
<b>Mode of Evaluation</b>	Experiment, Viva and Report
<b>Percentage of Weight</b>	13%







### Circuit Diagram

  

### Task

- Design of the digital circuit
- Implementation of the design
- Testing the circuit
- Report writing
  - Name of the experiment
  - Objective
  - Apparatus
  - Design of the circuit
    - Detail design methodology
    - Truth table (if required)
  - Circuit Diagram
  - Experimental data
  - Result and discussion
  - Precautions

Mode of Evaluation

Experiment, Viva and Report

Percentage of Weight

13%